

10K POTENTIOMETER

Potentiometers are variable resistors and they function to alter their resistance via a knob or dial. You have probably used one before by adjusting the volume on your stereo or using a light dimmer.


Potentiometers have a range of resistance. They can be attuned from zero ohms to whatever maximum resistance that is specific to it. For example, a potentiometer of 10 k Ω can be adjusted from 0 Ω to its maximum of 10 k Ω .

In this tutorial you will learn how to use a potentiometer with and without Arduino board to fade an LED.

You will also learn how to use `analogRead()` and `map()` functions.

TO USE POTENTIOMETER

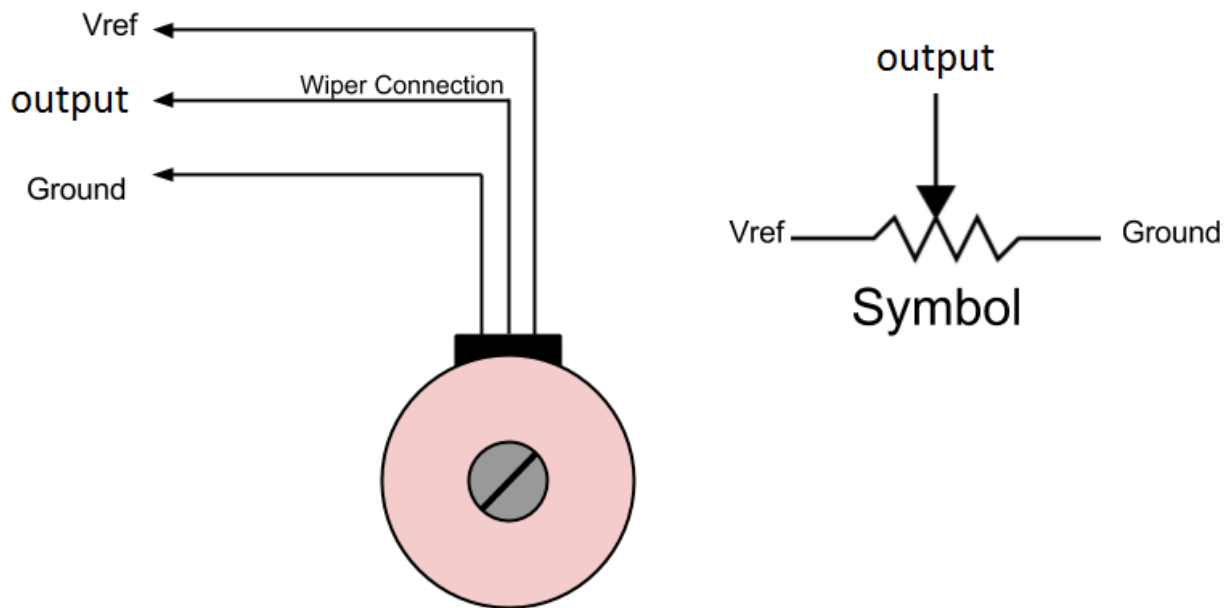Variable resistor / potentiometer Connection



All potentiometers have three pins. The outer pins are used for connecting power source (Vref and gnd). The middle pin (output) give us the variable of resistance value.

Let's see it in practice, you will need:


- potentiometer
- led
- battery AAA 1.5 (or another but no more than 5V)

Connect battery to outer pins of potentiometer and the positive end of led (larger pin) to middle pin. Now turn the knob (or dial) left and right.

It changes the brightness of the led!

Now let's see how we can connect the potentiometer with the arduino uno

CIRCUIT

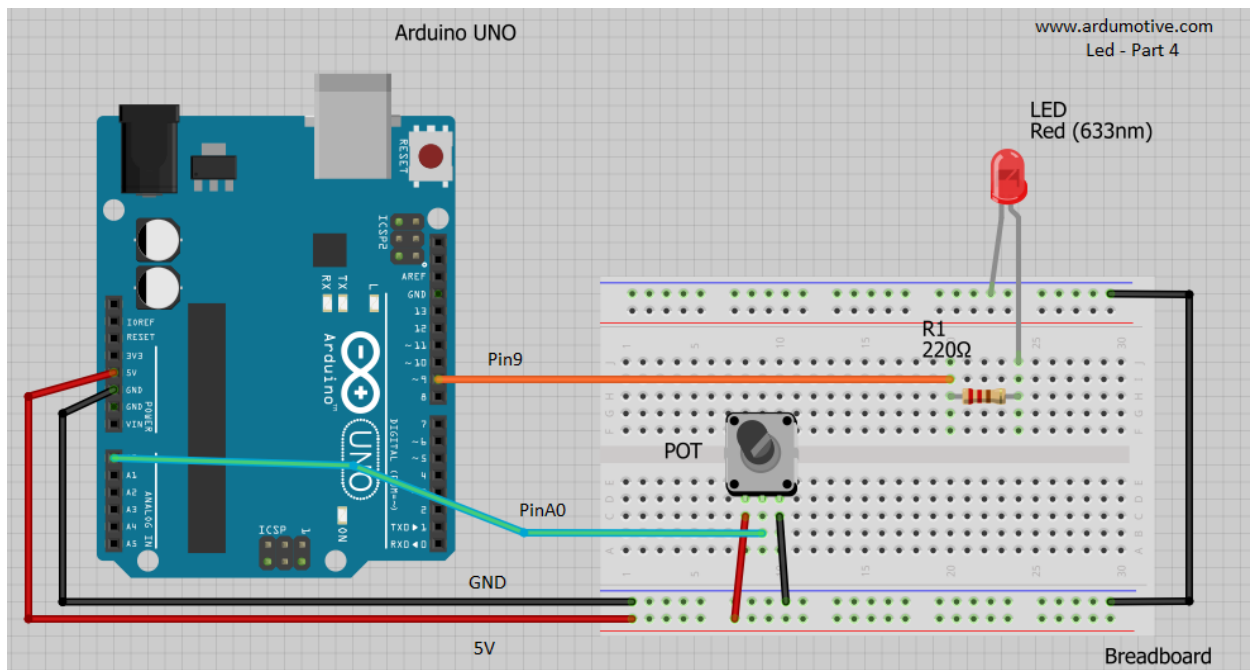

You will need:

- Arduino uno
- Breadboard
- LED
- 220 Ohm resistor
- Potentiometer (e.g. 4.7k)

CODE

Here's the 'Fade an LED with potentiometer' code, embedded using codebender!

By turning the shaft of the potentiometer, we change the amount of resistance on either side of the wiper which is connected to the center pin of the potentiometer. This changes the relative "closeness" of that pin to 5 volts and ground, giving us a different analog input. When the shaft is turned all the way in one direction, there are 0 volts going to the pin, and we read 0. When the shaft is turned all the way in the other direction, there are 5 volts going to the pin and we read 1023. In between, `analogRead()` returns a number between 0 and 1023 that is proportional to the amount of voltage being applied to the pin.

How it works:

Read analog value from potentiometer middle pin


-> `value=analogRead(potPin)`

Map analog values 0-1024 to pwm values 0-255

-> `value = map(value, 0, 1023, 0, 255);`

Send pwm value to led

-> `analogWrite(ledPin, value);`

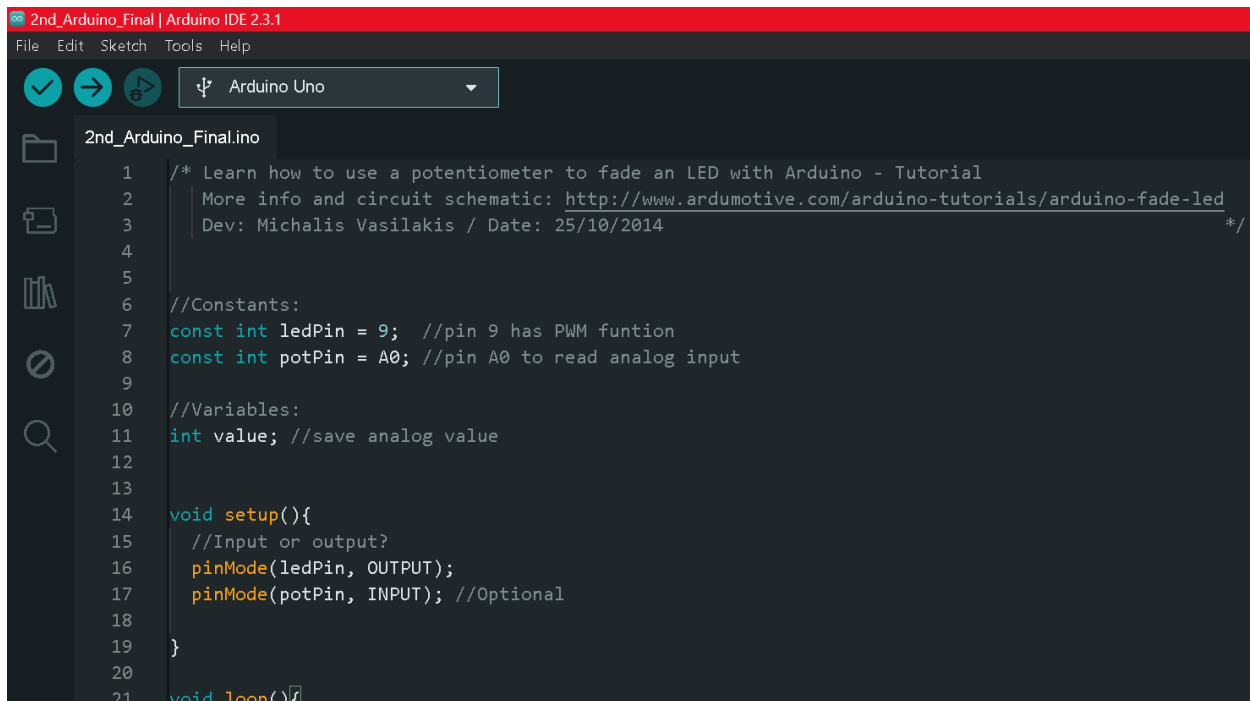

```
2nd_Arduino_Final | Arduino IDE 2.3.1
File Edit Sketch Tools Help
[Icons] Arduino Uno
2nd_Arduino_Final.ino
1  /* Learn how to use a potentiometer to fade an LED with Arduino - Tutorial
2     More info and circuit schematic: http://www.ardumotive.com/arduino-tutorials/arduino-fade-led
3     Dev: Michalis Vasilakis / Date: 25/10/2014 */
4
5
6  //Constants:
7  const int ledPin = 9; //pin 9 has PWM function
8  const int potPin = A0; //pin A0 to read analog input
9
10 //Variables:
11 int value; //save analog value
12
13
14 void setup(){
15     //Input or output?
16     pinMode(ledPin, OUTPUT);
17     pinMode(potPin, INPUT); //Optional
18 }
19
20
21 void loop(){
```

```
22
23   value = analogRead(potPin);           //Read and save analog value from potentiometer
24   value = map(value, 0, 1023, 0, 255); //Map value 0-1023 to 0-255 (PWM)
25   analogWrite(ledPin, value);           //Send PWM value to led
26   delay(100);                           //Small delay
27
28 }
```

REFERENCE:

<https://www.instructables.com/How-to-use-Potentiometer-Arduino-Tutorial/>